

# Boolean Function Oracles

## Introduction to Quantum Computing

Jothishwaran C.A.

Department of Electronics and Communication Engineering  
Indian Institute of Technology Roorkee

May 20, 2023

# Outline

## Qubits and Boolean strings

- Multi-qubit Basis

- $n$ -qubit operations revisited

## The Toffoli gate

- Definitions

- The circuit picture

## From classical gates to oracles

- The AND oracle

- Single bit oracles

## Defining Boolean Oracles

- The XOR oracle

- General Boolean Oracles

## Oracles as Quantum gates

- Some results

- A different oracle

# Boolean Strings as Basis Vectors

- ▶ A single-qubit computational basis vector can be represented as  $|x\rangle$ , where  $x \in \{0, 1\}$ .
- ▶ If there  $n$  such qubits, each with computational basis state  $|x_i\rangle$  where  $x_i \in \{0, 1\}$  and  $i \in [0, n - 1]$ .
- ▶ Computational basis vector for the  $n$ -qubit system can simply be defined as  $|x_0\rangle \otimes |x_1\rangle \otimes \cdots \otimes |x_{n-2}\rangle \otimes |x_{n-1}\rangle$ . There are  $2^n$  such vectors.
- ▶ Each of these basis vectors can now be represented as  $|x_0 x_1 \dots x_{n-1}\rangle \equiv |x\rangle$ , where  $x \in \{0, 1\}^n$ .
- ▶ This notation shall be adopted for defining multi-qubit basis vectors for all further discussions.

## The $X_n$ and $H_n$ gates

- ▶ If the  $X$  gate is applied to each of the  $n$  qubits of the system. The combined operator can be represented as:

$$\underbrace{X \otimes X \otimes \dots \otimes X}_{n\text{-times}} \equiv X^{\otimes n}$$

- ▶ When the  $H$  gate is applied to each of the  $n$  qubits of the system. The combined operator can be represented as:

$$\underbrace{H \otimes H \otimes \dots \otimes H}_{n\text{-times}} \equiv H^{\otimes n}$$

- ▶ When these operators are applied to the  $n$ -qubit basis state  $|0_n\rangle$  the results are as follows:

$$\begin{aligned} X^{\otimes n} |0_n\rangle &= |1_n\rangle \\ H^{\otimes n} |0_n\rangle &= \frac{1}{\sqrt{2^n}} \sum_{x \in \{0,1\}^n} |x\rangle \end{aligned}$$

# Toffoli gate: a formal introduction

- ▶ The Toffoli gate ( $CCX$ ) is a three qubit gate and has the following actions on the three-qubit computational basis:

$$CCX |000\rangle = |000\rangle ; CCX |100\rangle = |100\rangle$$

$$CCX |001\rangle = |001\rangle ; CCX |101\rangle = |101\rangle$$

$$CCX |010\rangle = |010\rangle ; CCX |110\rangle = |111\rangle$$

$$CCX |011\rangle = |011\rangle ; CCX |111\rangle = |110\rangle$$

- ▶ The matrix form is given as:

$$CCX = \begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \end{pmatrix}$$

# The Toffoli Circuit

- ▶ Combining the circuit conventions defined previously and the definitions of Boolean functions The circuit corresponding and the actions to the Toffoli gate is:

 


Figure 1: The Toffoli gate

- ▶ Here, each state  $|x_i\rangle$  is a computational basis vector for the single-qubit state.
- ▶ Since there were no phase factors in the actions defined before, the circuit also defines the resultant states for the input state vectors.

## A particular setup

- Consider the Toffoli gate with a condition the target qubit is initially fixed in the  $|0\rangle$  state:

 


Figure 2: The Toffoli gate

- The effect of the Toffoli gate on these initial states can be summarized as:

$$CCX |x_0\rangle |x_1\rangle |0\rangle = |x_0\rangle |x_1\rangle |x_0 \cdot x_1\rangle$$

# The AND Oracle

- ▶ The CCX gate with the initial state as shown before transforms the target qubit from  $|0\rangle$  to  $|x_0 \cdot x_1\rangle$
- ▶ Therefore for any initial control state represented by  $x_0x_1$  the circuit transforms the input state into the output state  $|x_0\rangle |x_1\rangle |x_0 \cdot x_1\rangle$
- ▶ This circuit is referred to as the Quantum AND Oracle: The circuit transforms an input state corresponding to the inputs of a classical AND gate, with a target qubit set to  $|0\rangle$  into an output state where the AND operation is performed and stored in the target qubit.
- ▶ The two-bit classical AND gate now has an equivalent three-qubit quantum oracle.



# Simpler Oracles

- ▶ If a two-bit classical gate has a three-qubit quantum oracle, then it maybe possible to define a single bit classical gate with a two-qubit oracle. Consider the following circuit:

 


Figure 3: A single bit oracle

- ▶ This is the equivalent oracle for the single bit function  $F(x) = x$ . The other single bit oracle maybe defined as follows:

 


Figure 4:  $F(x) = 0$

 


Figure 5:  $F(x) = 1$

 


Figure 6:  $F(x) = \bar{x}$

# Oracles with *CNOT* gates

- ▶ As discussed before, the *CNOT* gate acts on a two-qubit basis state  $|x_0\rangle |x_1\rangle$  as shown below

$$CNOT |x_0\rangle |x_1\rangle = |x_0\rangle |(x_0 + x_1)\rangle$$

- ▶ While this is equivalent to the XOR gate, it is not in the oracle form like the case with the *CCX* gate.
- ▶ However, consider the following circuit:

 


Figure 7: The XOR oracle

- ▶ This circuit is the three-qubit oracle equivalent to the classical XOR gate.

# Oracles with *CNOT* gates

- ▶ A general  $n$ -bit classical Boolean function has an equivalent  $(n + 1)$ -qubit quantum oracle representation  $U_F$  that acts as follows.

$$U_F |x\rangle |0\rangle = |x\rangle |F(x)\rangle$$

here,  $x \in \{0, 1\}^n$  and  $|x\rangle$  is an element of the  $n$ -qubit computational basis.

- ▶ The circuit representation of the same is as shown below. It should be noted that the upper bundle of qubit wires represent the  $n$ -qubit state.

 


Figure 8: The general quantum Boolean oracle

- ▶ It is possible to build any Boolean oracle with the *CNOT*, *CCX* and *X* gates.

# Varying the inputs of the Oracles

- ▶ Since the oracle is a unitary transformation, they are transformations since the inverse of  $U_F$  is simply the adjoint,  $U_F^\dagger$ .
- ▶ If the target qubit of an oracle is fixed to the  $|1\rangle$  state, then applying the oracle  $U_F$  on such a state yields the following:

$$U_F |x\rangle |1\rangle = |x\rangle |1 + F(x)\rangle$$

- ▶ The oracle is also, by its definition a linear transformation and so, if we consider a state  $|x_1\rangle + |x_2\rangle$  (normalization is disregarded) where  $x_1, x_2 \in \{0, 1\}^n$ . Then, applying  $U_F$  on this state gives:

$$U_F(|x_1\rangle + |x_2\rangle)|0\rangle = |x_1\rangle |F(x_1)\rangle + |x_2\rangle |F(x_2)\rangle$$

note that the separable input state may not be separable after  $U_F$  is applied.

- ▶ This is ability of a quantum oracle to evaluate multiple instances of the same function is a result of the linearity of the oracle. This feature is famously known as *Quantum Parallelism* and it has no classical equivalent.

## Varying the inputs of the Oracles

- ▶ If the target state of the qubit is set to the  $|-\rangle$  state, the action of  $U_F$  yields the following:

$$\begin{aligned}U_F |x\rangle |-\rangle &= U_F |x\rangle \frac{1}{\sqrt{2}}(|0\rangle - |1\rangle) \\&= |x\rangle \frac{1}{\sqrt{2}}(|0 + F(x)\rangle - |1 + F(x)\rangle)\end{aligned}$$

- ▶ The resultant target qubit is in the state  $|-\rangle$  when  $F(x) = 0$  and  $-|-\rangle$  when  $F(x) = 1$ . The combined result can be written as,

$$U_F |x\rangle |-\rangle = (-1)^{F(x)} |x\rangle |-\rangle$$

- ▶ In this case, it can be seen that the state of the target qubit is the same but the output state gains a phase that corresponds to the value of  $F(x)$ . This variation of the oracle is referred to as the Phase Oracle implementation of the Boolean function.