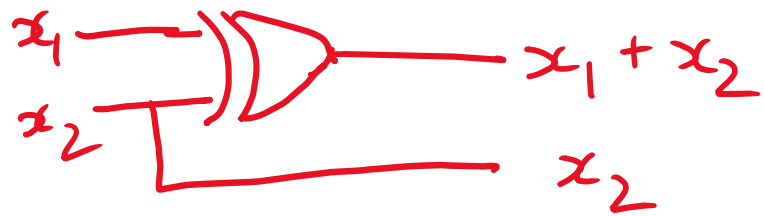


Reversible classical gates \Leftrightarrow We can know the input by observing the output

i) NOT gate

$x \rightarrow \neg x$: This is reversible by definition


ii) XOR gate (+)




x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	0

giving two-output bits
($x_1 + x_2$ & either of x_1 or x_2)
will make XOR reversible

AND gate (.)

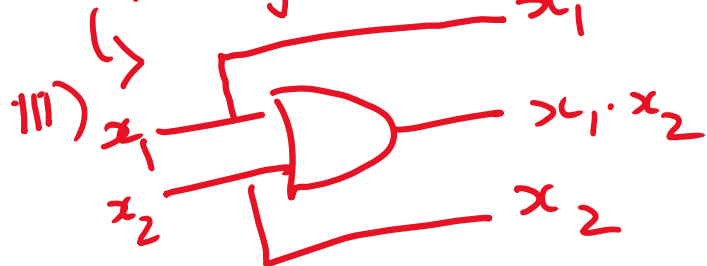

x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

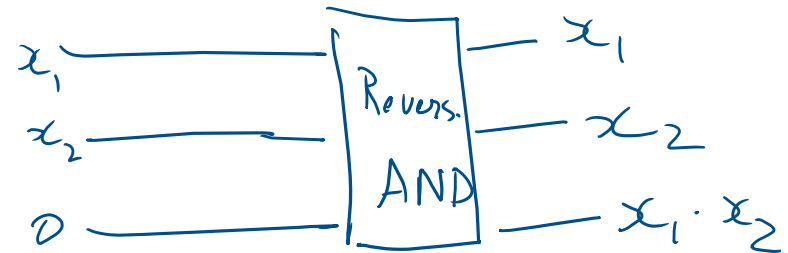

Correspondence between Reversible circuits & Quantum circuits

→ every Quantum gate is represented by a unitary matrix "U"


$$\therefore U \text{ is unitary} \Rightarrow U^\dagger U = U U^\dagger = I$$

$\dagger \equiv$ transposed conjugate

→ Every quantum gate operations are reversible

→ Every reversible classical circuit has a quantum analogue


Quantum version of reversible gates

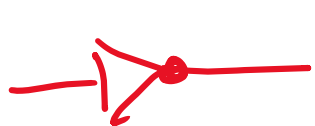


\equiv




X - gate

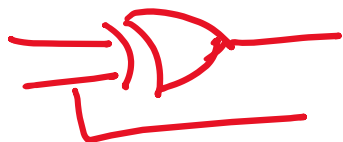


\equiv

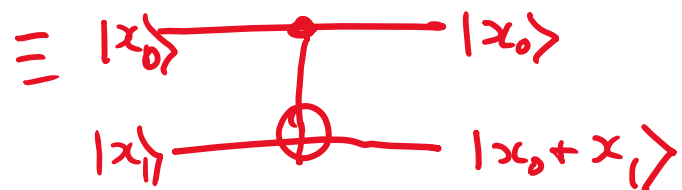

CNOT - gate

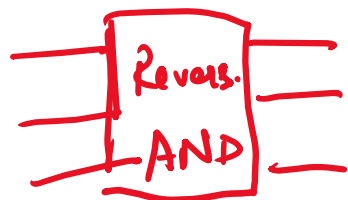

\equiv

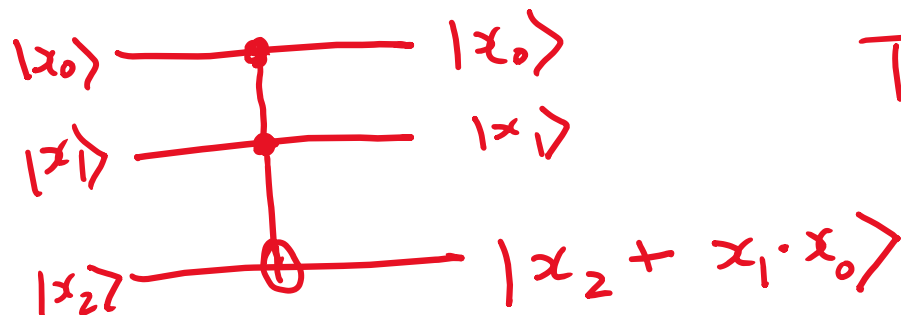

Toffoli gate

Construction of Bit Oracles (Quantum Oracles)

→ Given a Boolean function $F(x)$

→ construct a Quantum circuit for ^{evaluating} that Boolean f^n

i) The ANF (Algebraic normal form) of the function is given

$\{x_i\text{'s}, +, \cdot\}$

Ex: 1 construct an oracle for $F(x_0, x_1, x_2) = x_0 \cdot x_1 \cdot x_2$


Constructing the circuit for $x_0 \cdot x_1 \cdot x_2 = (x_0 \cdot x_1) \cdot x_2$

NOT - 1 bit
 XOR - 2 bit
 AND - 2 bit

XOR & AND are two-bit classical gates.

$U_F |x\rangle |0\rangle \rightarrow |x\rangle |F(x)\rangle$
 (no. of inputs) (output)

$3 + 1 = 4$ qubits

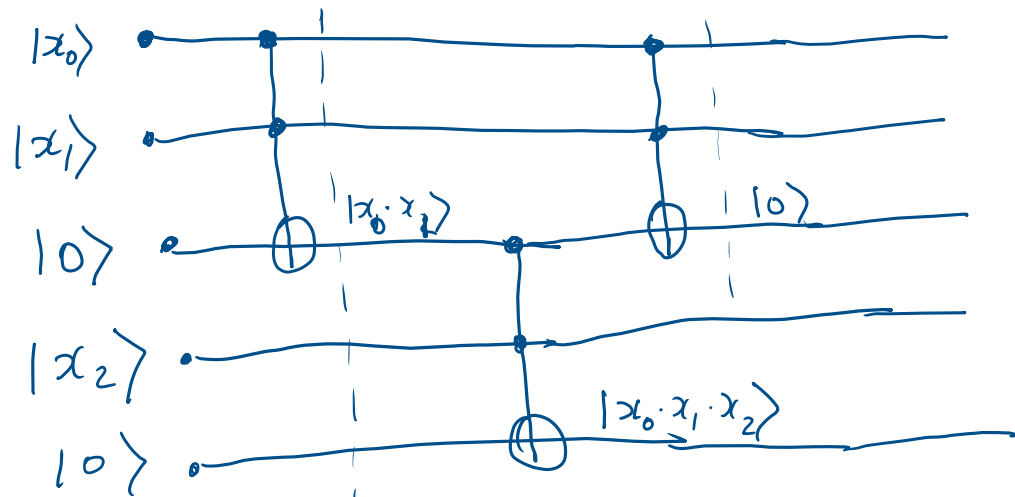

\Rightarrow Bit oracle for $x_0 \cdot x_1 \cdot x_2$

example $|x_0\rangle, |x_1\rangle = |11\rangle$

$(CX |11\rangle |0\rangle |0\rangle) \xrightarrow{CX} |11\rangle |1\rangle |0\rangle$

What about $CCCX$, $CCCCX$ and so on

→ Physical restriction : **only single and two-qubit transformations**
can be reliably applied

multi-input
AND gate



→ every high-degree terms in Boolean functions are
in practice we only up to toffoli gates.

$$x_0 x_1 x_2 x_3, \quad x_0 x_1 x_2$$